

 
 



Adaugarea de opcode-uri

MUX 4x1

 

MUXA 4x4

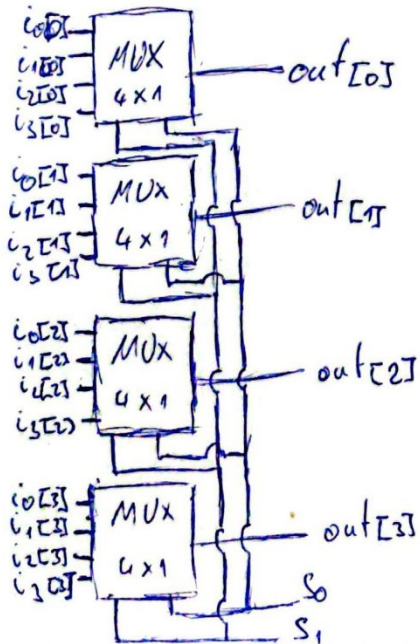

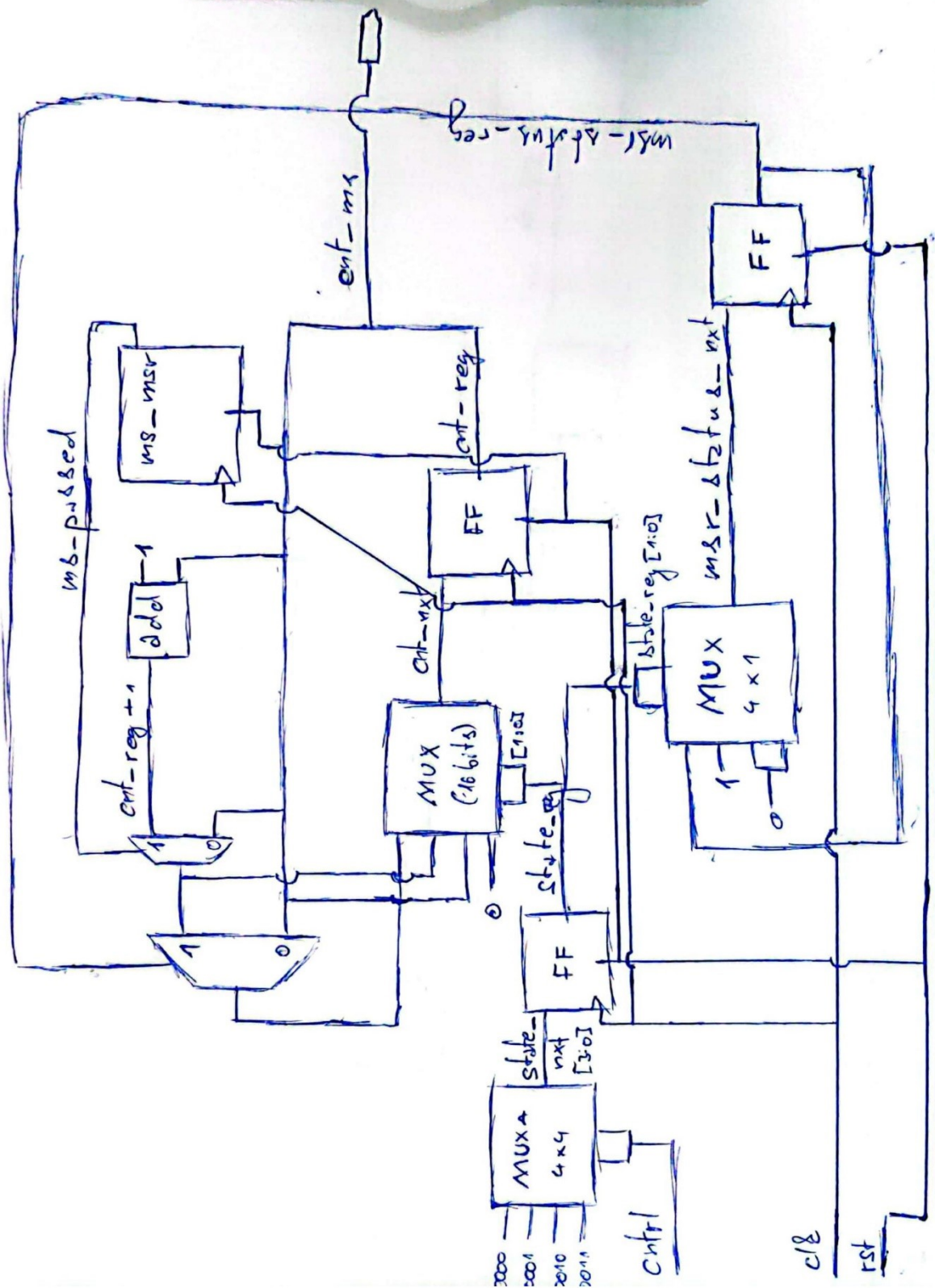

*MUXA 4x4 ar fi de fapt o implementare posibilă pentru “case”. În acest caz, primul bit este ignorat la ieşire.

Module:

```
module ms_cnt(
    input          clk, rst,
    input  [2:0]   cntrl,
    output [15:0]  cnt_ms
);

    reg  [15:0] cnt_reg, cnt_nxt;
    reg  [2:0]  state_reg, state_nxt;
    reg                msr_status_reg, msr_status_nxt;
    wire                ms_passed;
    wire [15:0] cnt_clk;

    localparam S0 = 3'b000;
    localparam S1 = 3'b001;
    localparam S2 = 3'b010;
    localparam S3 = 3'b011;

    ms_msr ms_msr_1(
        .clk(clk),
        .rst(rst),
        .ms_passed(ms_passed),
        .cnt_clk(cnt_clk)
    );

    always @(*) begin
        case(state_reg)
            S0: begin
```

```
if(msr_status_reg & ms_passed)
    cnt_nxt = cnt_reg + 1;
else
    cnt_nxt = cnt_reg;
end
```

```
S1: begin
    msr_status_nxt = 1;
    if(ms_passed)
        cnt_nxt = cnt_reg + 1;
    end
```

```
S2: begin
    msr_status_nxt = 0;
    cnt_nxt = cnt_reg;
end
```

```
S3: begin
    msr_status_nxt = 0;
    cnt_nxt = 0;
end
endcase
```

```
case(cntrl)
S0: begin
    state_nxt = S0;
end
```

```
S1: begin
```

```
    state_nxt = S1;  
end
```

```
S2: begin  
    state_nxt = S2;  
end
```

```
S3: begin  
    state_nxt = S3;  
end  
endcase
```

```
end
```

```
always @(negedge clk or posedge rst) begin
```

```
    if(rst == 1) begin
```

```
        cnt_reg <= 0;
```

```
        msr_status_reg <= 0;
```

```
        state_reg <= 0;
```

```
    end
```

```
    else begin
```

```
        cnt_reg <= cnt_nxt;
```

```
        msr_status_reg <= msr_status_nxt;
```

```
        state_reg <= state_nxt;
```

```
    end
```

```
end
```

```
assign cnt_ms = cnt_reg;
```

```
endmodule
```

Testbench:

```
//correct functionality for a timescale of 1ns/<precision>
```

```
module test;
```

```
initial begin
```

```
    $dumpfile("dump.vcd");
```

```
    $dumpvars(1, test);
```

```
end
```

```
reg                clk, rst;
```

```
reg  [2:0]  cntrl;
```

```
wire  [15:0] cnt_ms;
```

```
parameter period    =    200;           //200ns periods correspond to 5 MHz
```

```
parameter nr_p_s    =    5000;  //nr of periods in 1s
```

```
ms_cnt ms_cnt_1(
```

```
    .clk(clk),
```

```
    .rst(rst),
```

```
    .cnt_ms(cnt_ms),
```

```
    .cntrl(cntrl)
```

```
);
```

```
initial begin
```

```
    rst = 1;
```

```
    clk = 0;
```

```
    #10 rst = 0;
```

```
    cntrl = 3'b001;
```

```
end
```

```

initial begin
    repeat(80000)
        #(period/2) clk = ~clk;
end

```

```

initial begin
    #(2 * nr_p_s * period) cntrl = 3'b010;
    #(1 * nr_p_s * period) cntrl = 3'b001;
    #(1 * nr_p_s * period) cntrl = 3'b000;
    #(1 * nr_p_s * period) cntrl = 3'b011;
    #(1 * nr_p_s * period) cntrl = 3'b001;
end
endmodule

```

Functionality:

See waveform

